

Generic Carry Look Ahead

DUT:

Sum Block:

```
module Sum_blk #(
    parameter N = 4
) (
    input  logic [N - 1 : 0]    p_i    ,
    input  logic [N - 1 : 0]    cin    ,

    output logic [N - 1 : 0]    sum_o
);

    assign sum_o = p_i ^ cin ;
endmodule
```

G/P Generator:

```
module gp_gen #(
    parameter DATA_WIDTH = 4
) (
    input  logic [DATA_WIDTH-1:0] x_i    ,
    input  logic [DATA_WIDTH-1:0] y_i    ,

    output logic [DATA_WIDTH-1:0] g_o    ,
    output logic [DATA_WIDTH-1:0] p_o
);

    // Generate signals
    assign g_o = x_i & y_i ;

    // Propagate signals
    assign p_o = x_i ^ y_i ;
endmodule
```

4-Bit CLA:

```

module cla_4bit (
    input  logic cin      ,
    input  logic g0_i     ,
    input  logic p0_i     ,
    input  logic g1_i     ,
    input  logic p1_i     ,
    input  logic g2_i     ,
    input  logic p2_i     ,
    input  logic g3_i     ,
    input  logic p3_i     ,
    output logic c1_o     ,
    output logic c2_o     ,
    output logic c3_o     ,
    output logic c4_o     ,
    output logic p_o      ,
    output logic g_o      ,
);

    // Carry-out calculations
    assign c1_o = g0_i | (p0_i &
cin)
        ;

    assign c2_o = g1_i | (p1_i & g0_i) | (p1_i & p0_i &
cin)
        ;

    assign c3_o = g2_i | (p2_i & g1_i) | (p2_i & p1_i & g0_i) | (p2_i & p1_i & p0_i &
cin)
        ;

    assign c4_o = g3_i | (p3_i & g2_i) | (p3_i & p2_i & g1_i) | (p3_i & p2_i & p1_i &
g0_i) | (p3_i & p2_i & p1_i & p0_i & cin) ;

    // Group Propagate and Generate
    assign p_o = p3_i & p2_i & p1_i &
p0_i
        ;

    assign g_o = g3_i | (p3_i & g2_i) | (p3_i & p2_i & g1_i) | (p3_i & p2_i & p1_i &
g0_i) ;

endmodule

```

Top:

```

module CLA_top #(
    parameter int DATA_WIDTH = 64 // Width of the adder in bits (default 64-bit)
)(
    input logic [DATA_WIDTH-1:0] A, // First operand input
    input logic [DATA_WIDTH-1:0] B, // Second operand input
    input logic cin, // Carry input
    output logic [DATA_WIDTH-1:0] sum, // Sum output
    output logic cout // Carry output
);

// Calculate number of 4-bit groups needed (e.g., 64 bits / 4 = 16 groups)
localparam int NUM_GROUPS = DATA_WIDTH / 4;
// Calculate tree depth: log4(NUM_GROUPS) = log2(NUM_GROUPS)/2
// Each level combines 4 groups from previous level into 1 group
localparam int NUM_LEVELS = ($clog2(NUM_GROUPS)/2);

// Bit-level signals from initial GP generation
logic [DATA_WIDTH - 1 : 0] g_vector; // Generate: G[i] = A[i] & B[i] (both bits are 1)
logic [DATA_WIDTH - 1 : 0] p_vector; // Propagate: P[i] = A[i] ^ B[i] (carry will propagate through)

// Hierarchical group-level GP signals
// [NUM_LEVELS:0] represents levels 0 through NUM_LEVELS
// Level 0: 4-bit groups, Level 1: 16-bit groups, Level 2: 64-bit groups, etc.
logic [NUM_LEVELS : 0] g_group [NUM_GROUPS - 1 : 0]; // Group generate signals
logic [NUM_LEVELS : 0] p_group [NUM_GROUPS - 1 : 0]; // Group propagate signals

// Carry chain: carry_vector[i] is the carry into bit position i
logic [DATA_WIDTH:0] carry_vector;

// Generate bit-level G and P for all bit positions
// G[i] = A[i] & B[i]: this position generates a carry
// P[i] = A[i] ^ B[i]: this position will propagate an incoming carry
gp_gen #(
    .DATA_WIDTH(DATA_WIDTH)
) GP_GENERATOR (
    .x_i (A),
    .y_i (B),
    .g_o (g_vector),
    .p_o (p_vector)
);

// Initialize carry chain with input carry
assign carry_vector[0] = cin;

```

```

// ===== LEVEL 0: Process individual bits into 4-bit groups =====
// For 64-bit: creates 16 groups, each handling 4 consecutive bits
generate
  for (genvar i = 0 ; i < NUM_GROUPS ; i++) begin
    localparam int OFFSET = i * 4; // Starting bit index: 0, 4, 8, 12, ...
    logic c1, c2, c3, c4; // Intermediate carries within this 4-bit group

    // Each cla_4bit computes:
    // - Individual carries c1, c2, c3, c4 for bits within the group
    // - Group-level G and P that represent the entire 4-bit block
    // Group G = G3 | (P3&G2) | (P3&P2&G1) | (P3&P2&P1&G0)
    // Group P = P3 & P2 & P1 & P0
    cla_4bit gp4 (
      .cin(carry_vector[OFFSET]), // Carry into this 4-bit group
      .g0_i(g_vector[OFFSET]),    // Bit 0 generate
      .p0_i(p_vector[OFFSET]),    // Bit 0 propagate
      .g1_i(g_vector[OFFSET + 1]), // Bit 1 generate
      .p1_i(p_vector[OFFSET + 1]), // Bit 1 propagate
      .g2_i(g_vector[OFFSET + 2]), // Bit 2 generate
      .p2_i(p_vector[OFFSET + 2]), // Bit 2 propagate
      .g3_i(g_vector[OFFSET + 3]), // Bit 3 generate
      .p3_i(p_vector[OFFSET + 3]), // Bit 3 propagate
      .c1_o(c1), // Carry out of bit 0: C1 = G0 | (P0&Cin)
      .c2_o(c2), // Carry out of bit 1: C2 = G1 | (P1&G0) | (P1&P0&Cin)
      .c3_o(c3), // Carry out of bit 2
      .c4_o(c4), // Carry out of bit 3 (= carry out of entire 4-bit group)
      .p_o(p_group[0][i]), // Level 0 group propagate for group i
      .g_o(g_group[0][i])  // Level 0 group generate for group i
    );

    // Store computed carries back into the carry vector for sum calculation
    assign carry_vector[OFFSET + 1] = c1;
    assign carry_vector[OFFSET + 2] = c2;
    assign carry_vector[OFFSET + 3] = c3;
    assign carry_vector[OFFSET + 4] = c4; // This becomes carry input for next group
  end
endgenerate

// ===== LEVELS 1 to NUM_LEVELS: Build hierarchical CLA tree =====
// Each level combines 4 groups from the previous level into 1 parent group
// Level 1: combines 4-bit groups into 16-bit groups
// Level 2: combines 16-bit groups into 64-bit groups, etc.
generate
  for (genvar j = 1 ; j <= NUM_LEVELS ; j++) begin : levels
    // Number of child groups from previous level
    // Level 1: NUM_GROUPS/4^0 = 16 (for 64-bit)
    // Level 2: NUM_GROUPS/4^1 = 4
    // Level 3: NUM_GROUPS/4^2 = 1
    localparam int NUM_CHILD = (NUM_GROUPS / 4**(j - 1));

```

```

// Number of parent groups at this level
// Level 1: NUM_GROUPS/4^1 = 4 (16-bit groups)
// Level 2: NUM_GROUPS/4^2 = 1 (64-bit group)
localparam int NUM_PARENT = (NUM_GROUPS / 4**(j));
for (genvar k = 0; k < NUM_PARENT; k++) begin : parents
    // Index of first child group that feeds into this parent
    // Parent 0 uses children 0-3, Parent 1 uses children 4-7, etc.
    localparam int CHILD = k * 4;

    // Local GP signals for the 4 child groups
    logic g0, p0; // Child group 0
    logic g1, p1; // Child group 1
    logic g2, p2; // Child group 2
    logic g3, p3; // Child group 3

    // Fetch GP from child groups with bounds checking
    // If child doesn't exist (e.g., only 3 children), use default values
    // Default G=0 (no generate), P=1 (transparent propagate)
    assign g0 = (CHILD < NUM_CHILD) ? g_group[j - 1][CHILD] : 1'b0;
    assign p0 = (CHILD < NUM_CHILD) ? p_group[j - 1][CHILD] : 1'b1;
    assign g1 = (CHILD + 1 < NUM_CHILD) ? g_group[j - 1][CHILD + 1] : 1'b0;
    assign p1 = (CHILD + 1 < NUM_CHILD) ? p_group[j - 1][CHILD + 1] : 1'b1;
    assign g2 = (CHILD + 2 < NUM_CHILD) ? g_group[j - 1][CHILD + 2] : 1'b0;
    assign p2 = (CHILD + 2 < NUM_CHILD) ? p_group[j - 1][CHILD + 2] : 1'b1;
    assign g3 = (CHILD + 3 < NUM_CHILD) ? g_group[j - 1][CHILD + 3] : 1'b0;
    assign p3 = (CHILD + 3 < NUM_CHILD) ? p_group[j - 1][CHILD + 3] : 1'b1;

    // Combine 4 child groups into 1 parent group using CLA logic
    // Parent G = G3 | (P3&G2) | (P3&P2&G1) | (P3&P2&P1&G0)
    // Parent P = P3 & P2 & P1 & P0
    // No cin needed here - we're just combining GP signals, not computing carries
    cla_4bit COMB (
        .cin(1'b0), // Cin=0 for GP combination (not computing actual carries)
        .g0_i(g0),
        .p0_i(p0),
        .g1_i(g1),
        .p1_i(p1),
        .g2_i(g2),
        .p2_i(p2),
        .g3_i(g3),
        .p3_i(p3),
        .c1_o(), // Intermediate carries not needed - only final GP matters
        .c2_o(),
        .c3_o(),
        .c4_o(),
        .p_o(p_group[j][k]), // Parent group propagate
        .g_o(g_group[j][k]) // Parent group generate
    );
end
end
endgenerate

```

```
// Final carry out is the carry that would propagate beyond the last bit
assign cout = carry_vector[DATA_WIDTH];

// Compute final sum bits using: Sum[i] = P[i] ^ Carry[i]
// P[i] = A[i] ^ B[i], so Sum[i] = (A[i] ^ B[i]) ^ Carry[i] = A[i] ^ B[i] ^ Carry[i]
Sum_blk #(
    .N(DATA_WIDTH)
) SUM (
    .p_i    (p_vector),           // Bit-level propagate (A ^ B)
    .cin    (carry_vector[DATA_WIDTH-1:0]), // All carry signals (carry into each bit)
    .sum_o  (sum)                 // Final sum = (A ^ B) ^ Carry
);

endmodule
```

Verification:

Testbench:

```
module top_tb ();

    // Testbench parameter - can be overridden for different bit widths
    parameter DATA_WIDTH = 64;

    // DUT input signals
    logic [DATA_WIDTH-1:0] A;    // First operand for addition
    logic [DATA_WIDTH-1:0] B;    // Second operand for addition
    logic                  cin;  // Carry input

    // DUT output signals
    logic [DATA_WIDTH-1:0] sum;  // Sum result from CLA
    logic                  cout; // Carry output from CLA

    // Counters for test statistics
    int passed_tests = 0; // Count of successful test cases
    int failed_tests = 0; // Count of failed test cases

    // Expected result for comparison
    logic [DATA_WIDTH:0] expected_result; // Full width to hold sum + carry

endmodule
```

```

// Instantiate the Device Under Test (DUT)
CLA_top #(
    .DATA_WIDTH(DATA_WIDTH) // Pass parameterized width to CLA
) DUT (
    .A    (A),    // Connect operand A
    .B    (B),    // Connect operand B
    .cin  (cin),  // Connect carry input
    .sum  (sum),  // Connect sum output
    .cout (cout)  // Connect carry output
);

// Main test sequence
initial begin
    $display("=====");
    $display("Starting CLA Testbench");
    $display("Data Width: %0d bits", DATA_WIDTH);
    $display("=====\\n");

    // ===== Test 1: Corner Cases =====
    $display("Test 1: Corner Cases");

    // Test case 1a: All zeros (minimum values)
    A = 0; B = 0; cin = 0;
    #5; // Wait for combinational logic to settle
    check_result("All zeros");
    #5;

    // Test case 1b: All ones (maximum values, will overflow)
    A = '1; B = '1; cin = 1; // '1 creates all-ones pattern
    #5;
    check_result("All ones with carry");
    #5;

    // Test case 1c: Maximum value + 0
    A = '1; B = 0; cin = 0;
    #5;
    check_result("Max + 0");
    #5;

    // Test case 1d: Carry propagation test (alternating pattern)
    A = {DATA_WIDTH{1'b1}}; // All ones
    B = 1;                  // Add 1 to trigger full carry chain
    cin = 0;
    #5;
    check_result("Carry propagation chain");
    #5;

```



```

// ===== Test 2: Power-of-2 Values =====
$display("\nTest 2: Power-of-2 Values");

// Test addition of powers of 2 (single bit set)
for (int i = 0; i < DATA_WIDTH; i++) begin
    A = (1 << i); // 2^i
    B = 0;
    cin = 0;
    #5;
    check_result($sformatf("2^%0d", i));
    #5;
end

// ===== Test 3: Alternating Bit Patterns =====
$display("\nTest 3: Alternating Bit Patterns");

// Pattern: 0x5555... (01010101...)
A = {DATA_WIDTH{2'b01}};
B = {DATA_WIDTH{2'b10}}; // 0xAAAA... (10101010...)
cin = 0;
#5;
check_result("0x5555... + 0xAAAA...");
#5;

// Pattern: Same with carry
A = {DATA_WIDTH{2'b01}};
B = {DATA_WIDTH{2'b10}};
cin = 1;
#5;
check_result("0x5555... + 0xAAAA... + 1");
#5;

// ===== Test 4: Sequential Values =====
$display("\nTest 4: Sequential Additions");

// Test sequential numbers
for (int i = 0; i < 20; i++) begin
    A = i;
    B = i + 1;
    cin = i % 2; // Alternate carry input
    #5;
    check_result($sformatf("Sequential %0d", i));
    #5;
end

// ===== Test 5: Random Vectors =====
$display("\nTest 5: Random Test Vectors");

// Comprehensive random testing
repeat (1000) begin
    A = $random; // Generate random value for A

```

```

    B = $random;    // Generate random value for B
    cin = $random;  // Random carry input (0 or 1)
    #5;

    // Verify result matches expected sum
    check_result("Random");

    #5;
end

// ===== Test 6: Stress Test - Near Overflow =====
$display("\nTest 6: Near-Overflow Cases");

// Test values near maximum
for (int i = 0; i < 10; i++) begin
    A = ({DATA_WIDTH{1'b1}} - i); // Max - i
    B = i;
    cin = $random % 2;
    #5;
    check_result($sformatf("Near-max %0d", i));
    #5;
end

// ===== Final Report =====
$display("\n=====");
$display("Test Summary:");
$display("  Passed: %0d", passed_tests);
$display("  Failed: %0d", failed_tests);
$display("  Total:  %0d", passed_tests + failed_tests);

if (failed_tests == 0) begin
    $display("  Status: ALL TESTS PASSED ✓");
end else begin
    $display("  Status: SOME TESTS FAILED ✗");
end
end
$display("=====\\n");

$stop; // Stop simulation
end

```

```

// Task to check and report results
// Compares DUT output against expected value and updates statistics
task check_result(string test_name);
    // Calculate expected result: full width addition
    expected_result = A + B + cin;

    // Compare DUT output {cout, sum} with expected result
    if ({cout, sum} != expected_result) begin
        // Mismatch detected - report error
        $error("[%s] FAIL: A=%0h, B=%0h, cin=%0b => {cout,sum}=%0h, expected=%0h",
            test_name, A, B, cin, {cout, sum}, expected_result);
        failed_tests++;
    end else begin
        // Test passed
        $display("[%s] PASS: A=%0h + B=%0h + %0b = %0h",
            test_name, A, B, cin, {cout, sum});
        passed_tests++;
    end
endtask
endmodule

```

Waveform:

A	64d194251031	860...	1567726010		1787692501		461857079		321232678		1851723740		1062902654		1022176121		194251031
B	64d1844674407...	184...	792376158		18446744071782594074		1260861334		1844674407309388982		1130452870		18446744073400058075		18446744073661900026		18446744072920332449
cin	1'h0																
sum	64d1844674407...	184...	2360102168		18446744073570286576		1722718413		18446744073414621661		2982176610		753409114		974524532		18446744073114582480
cout	1'h0																
expected_result	65d1844674407...	1844674407336800...	2360102168		18446744073570286576		1722718413		18446744073414621661		2982176610		18446744074462960730		18446744074684076148		184467...




```


# =====
# Test Summary:
#   Passed: 1100
#   Failed: 0
#   Total: 1100
#   Status: ALL TESTS PASSED &
# =====
#
# ** Note: $finish      : CLA_tb.sv(166)
#   Time: 11 us  Iteration: 0  Instance: /top_tb
# 1
# Break in Module top_tb at CLA_tb.sv line 166


```

Vivado Results:


Elaboration:

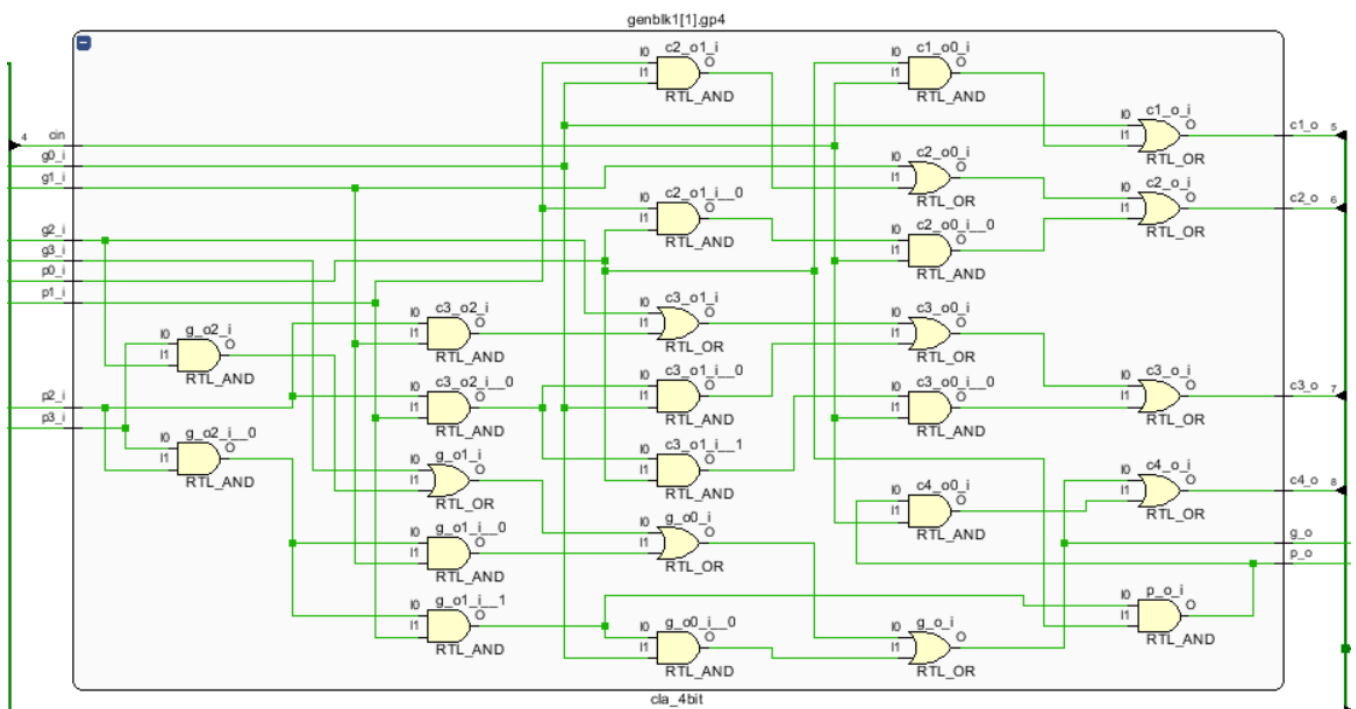 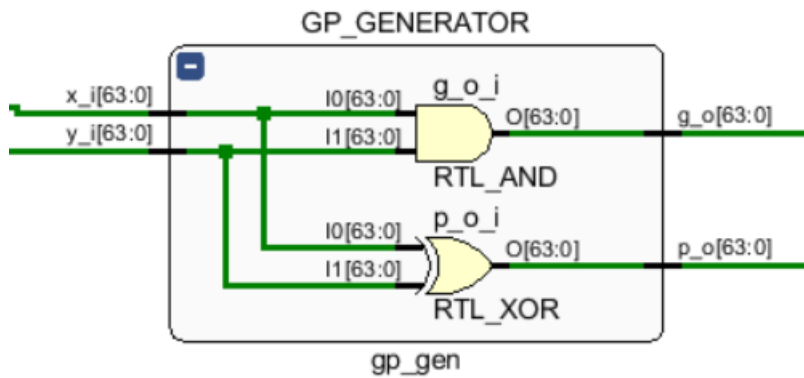

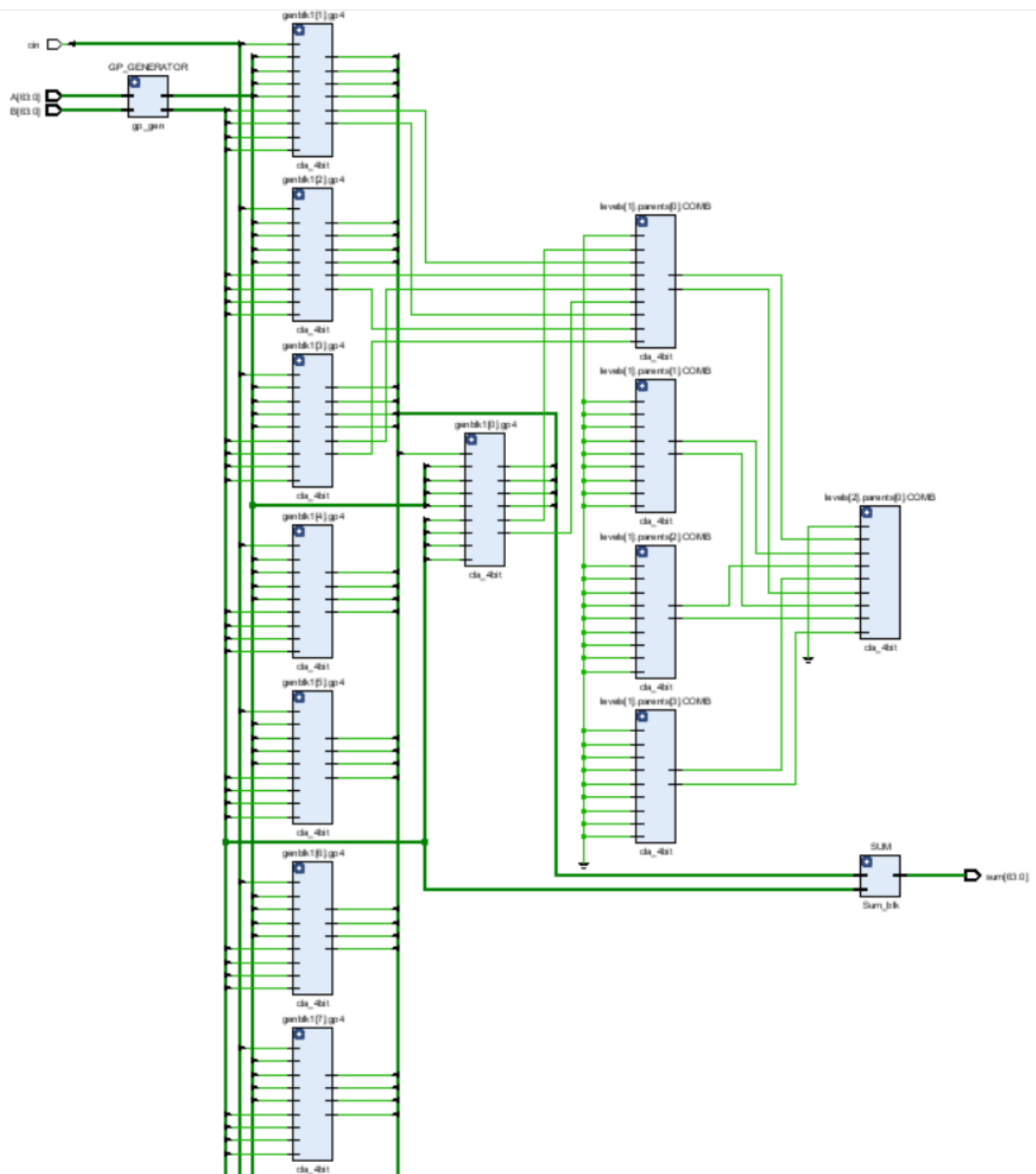

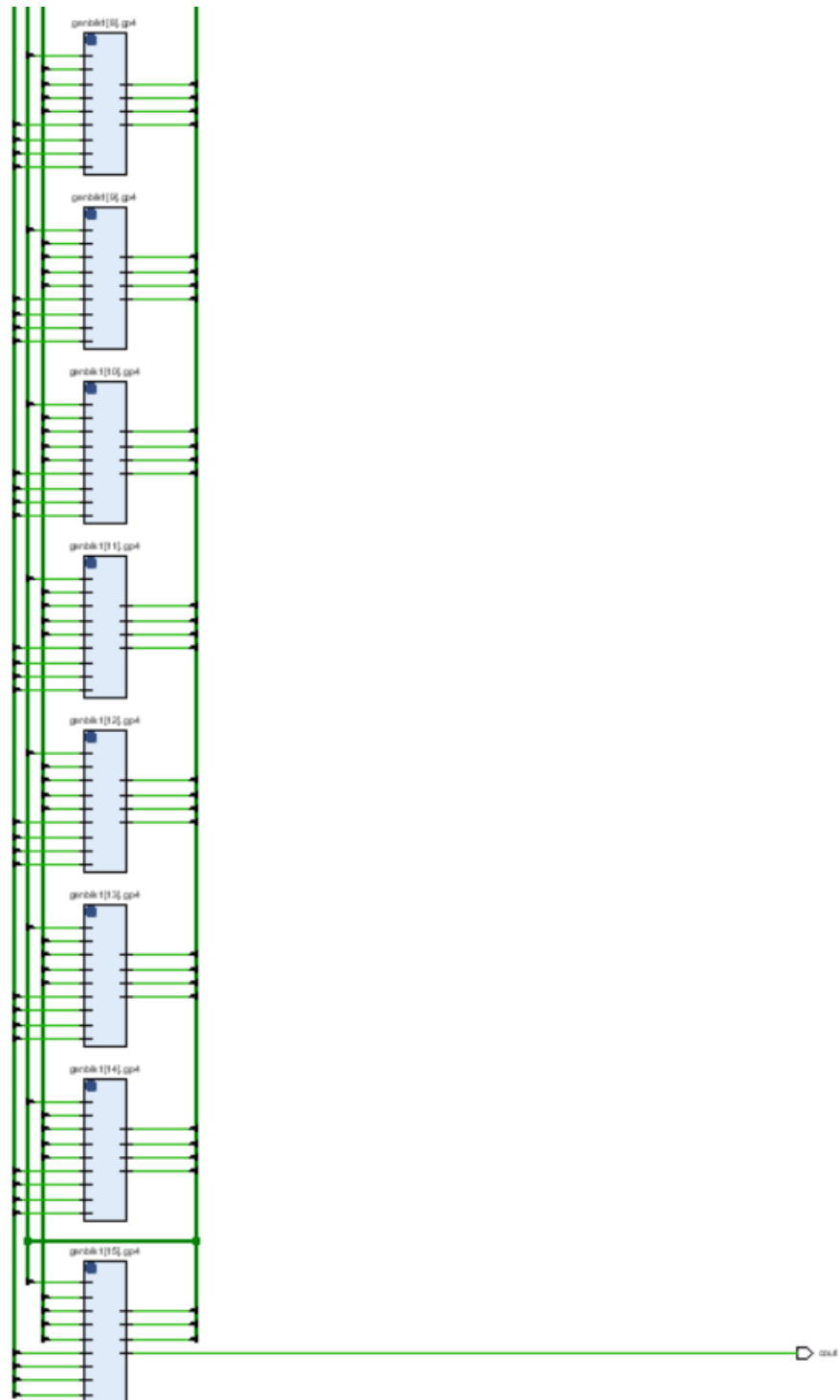


Synthesis:

 


Synthesis Utilization Analysis:

Summary

Resource	Utilization	Available	Utilization %
LUT	137	134600	0.10
IO	194	500	38.80

 

Implementation:

 


Implementation Utilization Analysis:

Name	1	Slice LUTs (134600)	Slice (33650)	LUT as Logic (134600)	Bonded IOB (500)
CLA_top		136	49	136	194

Summary

Resource	Utilization	Available	Utilization %
LUT	136	134600	0.10
IO	194	500	38.80

 

Limitations:

- Any value of the parameter “DATA_WIDTH” must be a logarithmic scale of 4 (e.g. 4, 16, 64, 256, ... etc.) otherwise the design will not work as expected.

Contacts:

- All code sources, with the latest updates, and analysis are provided in my GitHub [Mustafa11005/CLA_64_Bit](#)
- Email: elsherifmustafa04@gmail.com
- LinkedIn: [Mustafa EL-Sherif | LinkedIn](#)

Acknowledgments

[1] Computer arithmetic _ algorithms and hardware designs -- Parhami, Behrooz -- Oxford series in electrical and computer engineering, 2nd (Chapter 6)